

Digital Logic

Clock cycles begin on rising edge and gates provide delay

Combinational Logic: Adders, Multiplexor


Does not depend on itself, no loops

Updates are nearly instant

Sequential Logic: SR Latch, D-Latch, flip-flop, write to reg


State is dependent on itself, has loops

Has delay and updates on rising edge


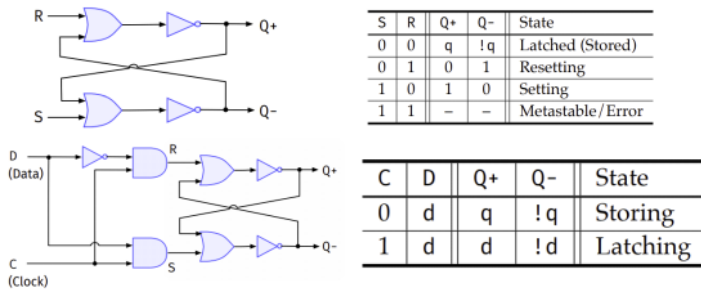


Microprocessor Design


Reg File

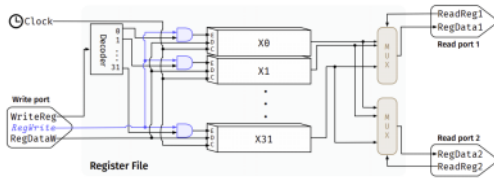


Memory

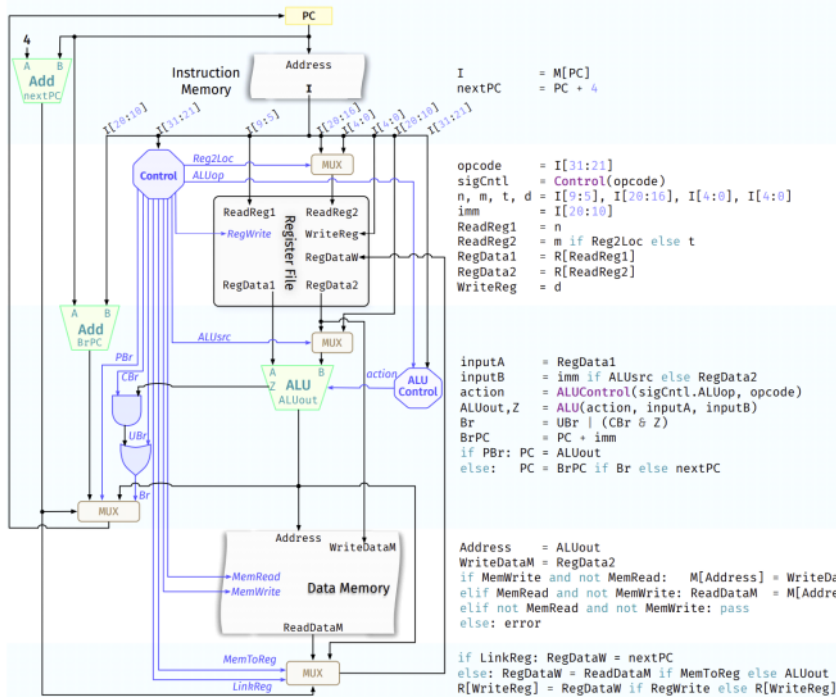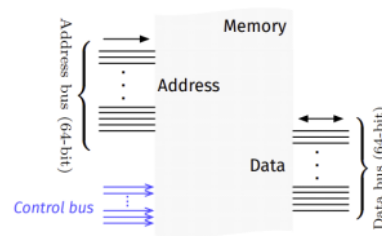

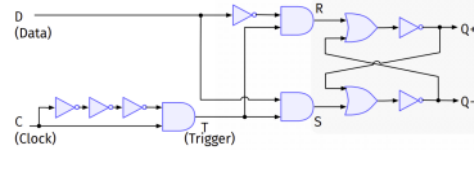
Multiplexor: to have more inputs must have $\lg N$ number of switch signal bits where N is the number of inputs



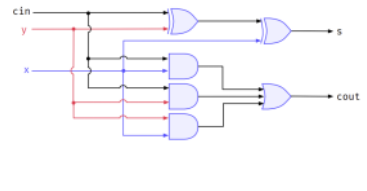Adder: Adds bits x and y together and if there is a carry then the cout is 1. Same for the cin




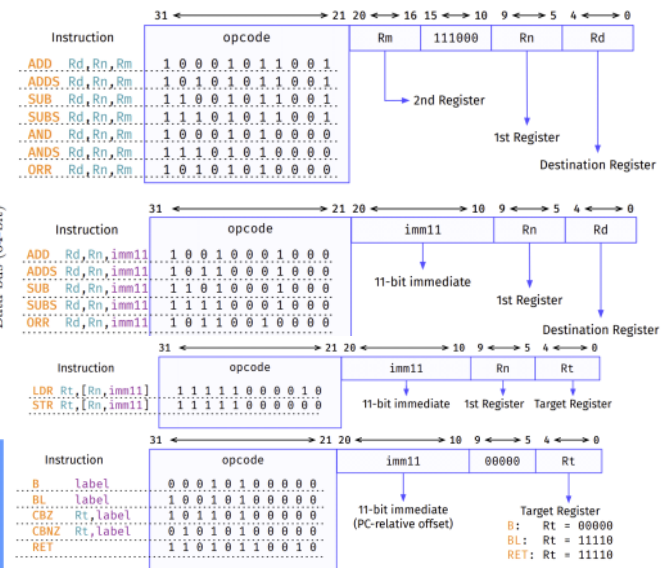Allows for output to change only when C is on the rising edge



ALUOp	action	ALU operation
AND	10 0000	ALUOut = inputA & inputB
ORR	10 0001	ALUOut = inputA inputB
SUB	10 0011	ALUOut = inputA - inputB
ADD	10 0100	ALUOut = inputA + inputB
LDR	00 0111	pass inputB, i.e., ALUOut = inputB
STR	00 0111	pass inputB, i.e., ALUOut = inputB
BL	01 0111	pass inputB, i.e., ALUOut = inputB
CBZ	01 0111	pass inputB, i.e., ALUOut = inputB
CBNZ	01 0111	pass inputB, i.e., ALUOut = inputB
RET	01 0111	pass inputB, i.e., ALUOut = inputB
ANDS	11 1000	ALUOut = inputA & inputB (set Z)
ADDs	11 1010	ALUOut = inputA + inputB (set Z)
SUBs	11 1011	ALUOut = inputA - inputB (set Z)

IF ID EX ME WB

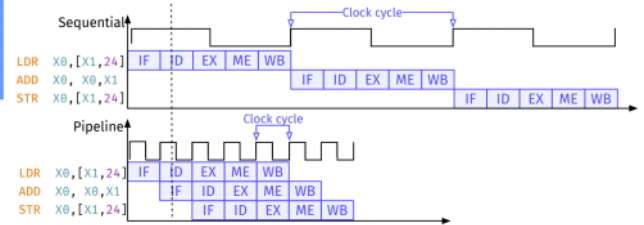

- (IF) Instruction Fetching:** the instruction is obtained from memory;
- (ID) Instruction Decoding:** the fetched instruction will pass different fields to different data signals, and the opcode will be used for converting into control signals. Register data will also be read;
- (EX) Execution:** ALU will perform the operation based on the decoded instruction, and produce the result;
- (ME) Memory Access:** Sending data to memory or reading data from memory;
- (WB) Writing Back:** Write result back to register.

In none Pipe:

CC: sum of all stages

Latency: sum of all stages

In Pipelined:

CC: length of longest stage

Latency: number of stages multiplied by the CC